

Introduction to Efficient and Secure Arithmetic Circuits

Arnaud TISSERAND

CNRS, Lab-STICC

Conférence rentrée informatique ENS Paris-Scalay. Sept. 2021



Course Language

Slides have been prepared in *English*.

Some words/remarks are also given in FR *French* in case of not immediate translation or specific feature.

Questions, comments and help requests are welcome in both French and English.

Licence

This document is licensed under a Creative Commons Attribution - NonCommercial 4.0 International License.

<https://creativecommons.org/licenses/by-nc/4.0/>

All figures and tables not from the author are presented with their [source](#).

Summary

Computer Arithmetic

Preliminaries on Digital Circuits

Addition & Multiplication

Introduction to Physical Attacks

Protections at the Arithmetic Level

References

References to books, articles and links are given throughout and at the end of this document.

Computer Arithmetic

What is Computer Arithmetic? (Personal Definition)

Branch of *computer engineering/science* that deals with:

- **representations** of **numbers**: formats, coding and behavior for (subsets of) \mathbb{N} , \mathbb{Z} , \mathbb{Q} , \mathbb{R} , \mathbb{C} , \mathbb{F}_q , \dots , fixed vs multiple precision;
- **algorithms** for **operations**: \pm , \times , \div , $\sqrt{\quad}$, $\frac{1}{x}$, $\frac{1}{\sqrt{x}}$, $\frac{1}{\sqrt{x^2+y^2}}$, \exp , \log , \sin , \cos , mod , gcd , $(a + b) \text{ mod } p$, conversions, \dots ;
- **implementations** in **hardware** or(/and) **software**;
- **quality**: error/accuracy, specific cases (div. by 0), reproducibility;
- **speed**: delay, latency, throughput;
- **costs**: silicon area, code/data memory, power/energy consumption;
- **methods and tools**: study, coding, validation, verification, porting, evaluation, \dots ;
- **training** of programmers and users;
- ?

Computer Arithmetic Overview

representations
of numbers

$\mathbb{N}, \mathbb{Z}, \mathbb{Q}, \simeq \mathbb{R}, \mathbb{F}_q$

algorithms

$\pm, \times, \div, \sqrt{}, \text{mod},$
 $\forall, \leq, e^x, \simeq f(x), \dots$

Computer Arithmetic Overview

representations
of numbers

$\mathbb{N}, \mathbb{Z}, \mathbb{Q}, \simeq \mathbb{R}, \mathbb{F}_q$

algorithms

$\pm, \times, \div, \sqrt{}, \text{mod},$
 $\forall, \leq, e^x, \simeq f(x), \dots$

implementation

soft GPP/SP,
ASIC, FPGA

Computer Arithmetic Overview

representations
of numbers

$\mathbb{N}, \mathbb{Z}, \mathbb{Q}, \simeq \mathbb{R}, \mathbb{F}_q$

algorithms


$\pm, \times, \div, \sqrt{}, \text{mod},$
 $\forall, \exists, e^x, \simeq f(x), \dots$

implementation

soft GPP/SP,
ASIC, FPGA

application



Computer Arithmetic Overview

 


implementation
soft GPP/SP,
ASIC, FPGA

application


Computer Arithmetic Overview

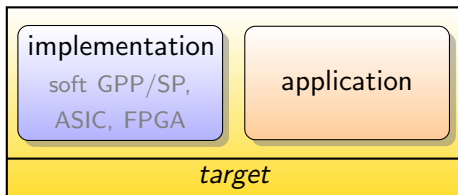 


Computer Arithmetic Overview

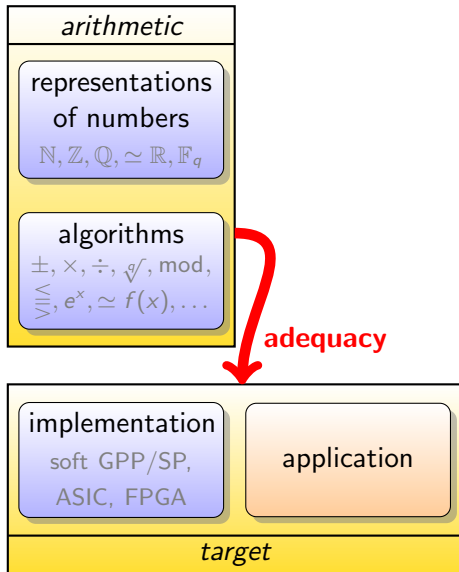

Computer Arithmetic Overview

 

adequacy

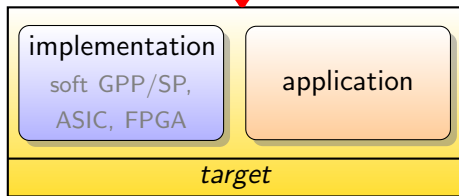

accuracy
behavior
test, simulation
proof, formal method

validation

a priori

a posteriori

speed, throughput, latency


circuit area
memory (I and D)
energy, power
security, reliability

performances

modelling

measurement

Computer Arithmetic Overview

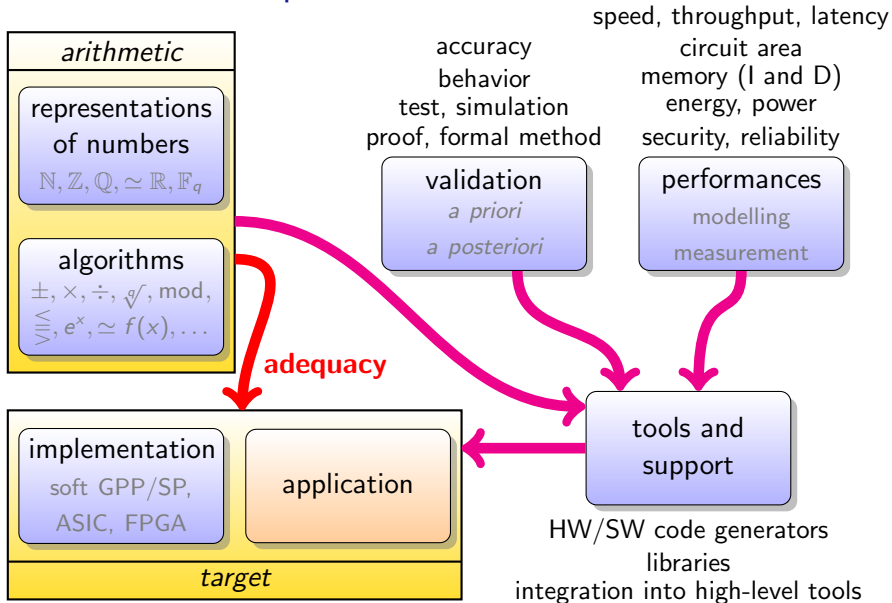

Computer Arithmetic Close Domains

- microelectronics for digital circuits;
- computer architecture for processor design (units, instructions, registers, interruptions, counters . . .);
- programming languages and compilation;
- numerical computing and applied mathematics;
- formal proofs and verification methods;
- computer algebra (\mathbb{FR} *calcul formel*);
- specific application domains such as signal and image processing, AI
- and probably other domains. . .

Computer Arithmetic in Software (Example SW1)

The following Python code:

```
a, b = 1, 9
c = a + b
print(c, type(c))

from math import *
x = pi + 1.0
print(x, type(x))

print([ sin(pi/n) for n in [4, 6, 12] ])
```

produces (using Python 3.7):

```
10 <class 'int'>
4.141592653589793 <class 'float'>
[0.7071067811865475, 0.49999999999999994, 0.25881904510252074]
```

Warning: do not perform *large* computations using “raw” Python, use NumPy standard library (see also Numba or PyPy)!

Computer Arithmetic in Software (Example SW2)

The following C code:

```
#include <stdio.h>
#include <math.h>

int main() {
    double n = 4.0;
    double x = M_PI;
    double y = sin(x/n);
    printf("y = %f\n", y);
    return 0;
}
```

compiled (gcc 8.3) using:

```
gcc -lm example_sin.c
```

produces:

```
y = 0.707107
```

Computer Arithmetic in Software (Example SW3)

The following Python code:

```
a = 1.0
b = 12.345e50
c = 9.8765e-40
v = [a, -a, b, -b, c, -c]
print(sum(v))

from itertools import permutations
print(sorted(set( [ sum(e) for e in permutations(v) ] )))
```


produces (using Python 3.7):

```
0.0
[-1.0, -9.8765e-40, 0.0, 9.8765e-40, 1.0]
```

Warning: associativity does not (necessarily) hold for floating-point arithmetic! See for instance: *David Goldberg. What every computer scientist should know about floating-point arithmetic. ACM Comput. Surv. 23, March 1991, DOI: <https://doi.org/10.1145/103162.103163>*

Computer Arithmetic in Hardware (Example HW1)

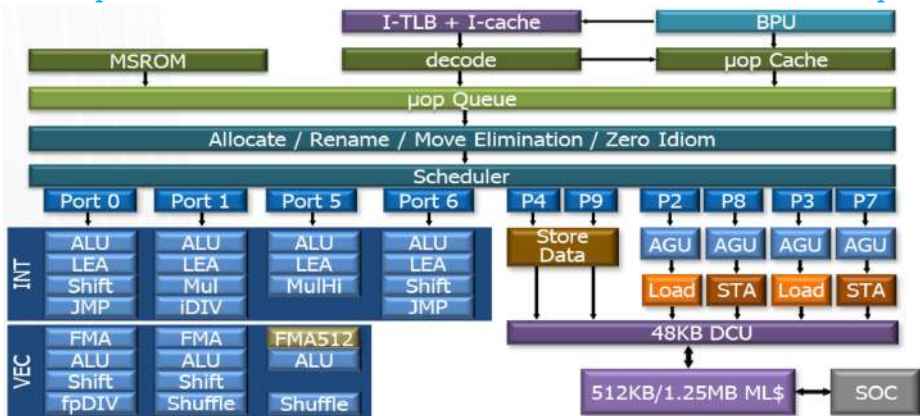Overview of one core in an Intel Xeon processor, source: https://www.hc32.hotchips.org/assets/program/conference/day1/HotChips2020_Server_Processors_Intel_Irma_ICX-CPU-final3.pdf



Link to other examples: <https://en.wikichip.org/wiki/WikiChip>

Computer Arithmetic in Hardware (Example HW2)

Source: *NVIDIA TURING GPU ARCHITECTURE* white paper (WP-09183-001_v01)





See also: <https://developer.nvidia.com/blog/nvidia-turing-architecture-in-depth/>



Preliminaries on Digital Circuits

Logic Values: Representation

The logic values $\{0, 1\}$ are represented using **voltages**:

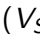- $0 \iff$ reference voltage or **ground** (V_{SS} , )
- $1 \iff$ **supply voltage** ($V_{DD} > 0$ or )

 
 
Due to the noise in the circuit (from many sources), the logic values must be represented using **voltage intervals** (noise margins): **digital** vs. **analog**



CMOS Logic


CMOS = *complementary MOS*

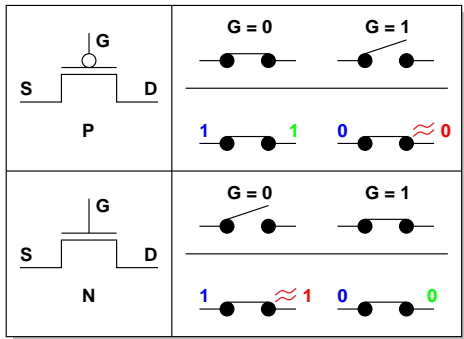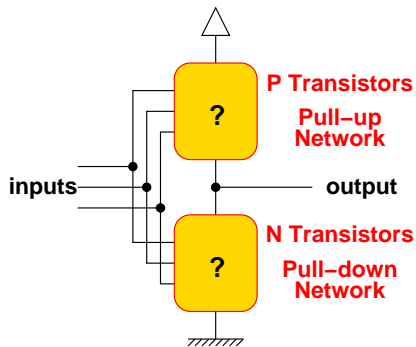N and P transistors are only used for passing **strong** signals




Logic Gate: Inverter

 The simplest gate: only 2 transistors (1 N and 1 P)




A	Y
0	1
1	0


circuit:

 


behavior:

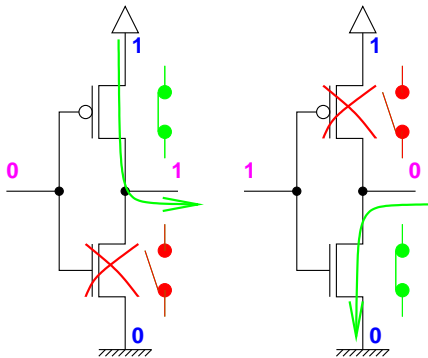


Logic Gate: NAND2 (2-input not-and)

 


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 

Logic Gate: NAND3 (3-input NAND)

 



A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 

The number of transistors in **series** is **limited** (3 to 5)

Memory Elements

  
There are many types of memory elements. Here, we will only focus on standard **flip-flops**




CLK	D	Q(t+1)	Q \bar{N} (t+1)
1	X	Q(t)	Q \bar{N} (t)
0	X	Q(t)	Q \bar{N} (t)
\uparrow	0	0	1
\uparrow	1	1	0

Remark:

\uparrow is the rising clock **edge**

 




Setup, Hold and Propagation Delays

 

- **setup** delay (t_{setup}): data should be held steady *before* clock edge
- **hold** delay (t_{hold}): data should be held steady *after* clock edge
- **propagation** delay (t_{propag}): propagation time from D to Q

Fanout ($\boxed{\text{FR}}$ *sortance*)

   The gate **delay** (change output state) depends on the **output load**. **Fanout** measures this load as the number of inputs of gate connected to the output (normalized w.r.t. an inverter)



Power Consumption: Basic Definitions

Instantaneous power:

$$P(t) = i_{DD}(t) V_{DD}$$

Energy over some time interval T:


$$E = \int_0^T i_{DD}(t) V_{DD} dt$$

Average power over interval T:

$$P_{avg} = \frac{E}{T} = \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt$$

Units:

 - current A
- voltage V
- power W
- energy J or Wh



Power Consumption: Components


Power dissipation in CMOS circuits comes from 2 main components:

- **static** dissipation:
 - ▶ sub-threshold conduction through OFF transistors
 - ▶ leakage current through P-N junctions
 - ▶ tunneling current through gate oxide
 - ▶ ...
- **dynamic** dissipation:
 - ▶ charging and discharging of load capacitances (useful + parasitic)
 - ▶ short-circuit current

$$P_{\text{total}} = P_{\text{static}} + P_{\text{dynamic}}$$

Charging and Discharging Load Capacitances

 There are capacitances **everywhere** in the circuit: transistor gate, routing, parasitics. . .



Solutions:

- design **small** circuits (small transistor, short wires, technology shrinking)
- **reduce the activity** (algorithms, data coding, sleep mode)
- **reduce** V_{DD} (without lowering speed)

Simple Power Consumption Model

Average **dynamic power dissipation** (no leakage, no short circuit):

$$P = \alpha \times C \times f \times V_{DD}^2$$


where

- α is the activity factor
- C is the average switched capacitance (at each cycle)
- f is the circuit frequency
- V_{DD} is the supply voltage


Remark: the gate delay is $d = \gamma \times \frac{C \times V_{DD}}{(V_{DD} - V_T)^2} \approx \frac{1}{V_{DD}}$

Power Reduction at Gate Level

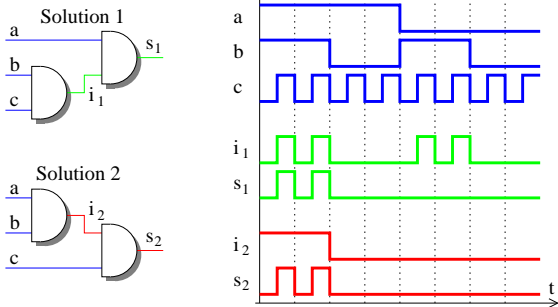- gate and/or input reordering (reduce glitching power):



 - use complex gates (reduce internal capacitances and area):



Addition & Multiplication

Positional Number System(s)

$$X = \sum_{i=-m}^{n-1} x_i \beta^i = (x_{n-1}x_{n-2} \cdots x_1x_0 \cdot x_{-1}x_{-2} \cdots x_{-m})$$

- **radix** β (usually a power of 2)
- **digits** x_i ($\in \mathbb{N}$) in the **digit set** \mathcal{D}
- **rank** or **position** i , **weight** β^i
- n **integer** digits, m **fractional** digits

Examples:

- $\beta = 10, \mathcal{D} = \{0, 1, 2, 3, 4, 5, 6, 7, 8, 9\}$
- $\beta = 2, \mathcal{D} = \{0, 1\}$

Positional Number System(s)

$$X = \sum_{i=-m}^{n-1} x_i \beta^i = (x_{n-1}x_{n-2} \cdots x_1x_0 \cdot x_{-1}x_{-2} \cdots x_{-m})$$

- **radix** β (usually a power of 2)
- **digits** x_i ($\in \mathbb{N}$) in the **digit set** \mathcal{D}
- **rank** or **position** i , **weight** β^i
- n **integer** digits, m **fractional** digits

Examples:

- $\beta = 10, \mathcal{D} = \{0, 1, 2, 3, 4, 5, 6, 7, 8, 9\}$
- $\beta = 2, \mathcal{D} = \{0, 1\}$
- carry save: $\beta = 2, \mathcal{D}_{\text{cs}} = \{0, 1, 2\}$
- borrow save: $\beta = 2, \mathcal{D}_{\text{bs}} = \{-1, 0, 1\}$

Positional Number System(s)

$$X = \sum_{i=-m}^{n-1} x_i \beta^i = (x_{n-1}x_{n-2} \cdots x_1x_0 \cdot x_{-1}x_{-2} \cdots x_{-m})$$

- **radix** β (usually a power of 2)
- **digits** x_i ($\in \mathbb{N}$) in the **digit set** \mathcal{D}
- **rank** or **position** i , **weight** β^i
- n **integer** digits, m **fractional** digits

Examples:

- $\beta = 10, \mathcal{D} = \{0, 1, 2, 3, 4, 5, 6, 7, 8, 9\}$
- $\beta = 2, \mathcal{D} = \{0, 1\}$
- carry save: $\beta = 2, \mathcal{D}_{cs} = \{0, 1, 2\}$
- borrow save: $\beta = 2, \mathcal{D}_{bs} = \{-1, 0, 1\}$
- signed digits: $\beta > 2, \mathcal{D}_{sd,\alpha,\beta} = \{-\alpha, \dots, \alpha\}$ with $2\alpha + 1 \geq \beta$

Positional Number System(s)

$$X = \sum_{i=-m}^{n-1} x_i \beta^i = (x_{n-1}x_{n-2} \cdots x_1x_0 \cdot x_{-1}x_{-2} \cdots x_{-m})$$

- **radix** β (usually a power of 2)
- **digits** x_i ($\in \mathbb{N}$) in the **digit set** \mathcal{D}
- **rank** or **position** i , **weight** β^i
- n **integer** digits, m **fractional** digits

Examples:

- $\beta = 10, \mathcal{D} = \{0, 1, 2, 3, 4, 5, 6, 7, 8, 9\}$
- $\beta = 2, \mathcal{D} = \{0, 1\}$
- carry save: $\beta = 2, \mathcal{D}_{cs} = \{0, 1, 2\}$
- borrow save: $\beta = 2, \mathcal{D}_{bs} = \{-1, 0, 1\}$
- signed digits: $\beta > 2, \mathcal{D}_{sd,\alpha,\beta} = \{-\alpha, \dots, \alpha\}$ with $2\alpha + 1 \geq \beta$
- theoretical systems: $\beta = \frac{1+\sqrt{5}}{2}, \beta = 1 + i \dots$

Radix-2 Signed Integers

- sign and magnitude (absolute value)

$$A = (s_a a_{n-2} \dots a_1 a_0) = (-1)^{s_a} \times \sum_{i=0}^{n-2} a_i 2^i$$

- 2's complement

$$A = (a_{n-1} a_{n-2} \dots a_1 a_0) = -a_{n-1} 2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i$$

- biased (usually $B = 2^{n-1} - 1$)

$$A = A_{math} + B$$


- ...

Signed Integers

integer	representations		
	sign/magnitude	2's complement	biased (B=7)
-8	---	1000	---
-7	1111	1001	0000
-6	1110	1010	0001
-5	1101	1011	0010
-4	1100	1100	0011
-3	1011	1101	0100
-2	1010	1110	0101
-1	1001	1111	0110
0	0000	0000	0111
1	0001	0001	1000
2	0010	0010	1001
3	0011	0011	1010
4	0100	0100	1011
5	0101	0101	1100
6	0110	0110	1101
7	0111	0111	1110
8	---	---	1111

Fixed-Point Representations

 Widely used in DSPs and digital integrated circuits for higher speed, lower silicon area and power consumption compared to floating point



Typical fixed-point formats: 16, 24, 32 and 48 bits

Floating-Point Representation(s)

Radix- β floating-point representation of x :

- **sign** s_x , 1-bit encoding: $0 \Rightarrow x > 0$ and $1 \Rightarrow x < 0$
- **exponent** $e_x \in \mathbb{N}$ on k digits and $e_{min} \leq e_x \leq e_{max}$
- **mantissa** m_x on $n + 1$ digits
- encoding:

$$x = (-1)^{s_x} \times m_x \times \beta^{e_x}$$

$$m_x = x_0 . x_1 x_2 x_3 \cdots x_n$$

$$x_i \in \{0, 1, \dots, \beta - 1\}$$


For accuracy purpose, the mantissa must be **normalized** ($x_0 \neq 0$)

Then $m_x \in [1, \beta[$ and a specific encoding is required for the number 0

IEEE-754: basic formats

Radix $\beta = 2$, the first bit of the normalized mantissa is always a “1” (non-stored implicit bit)

format	number of bits			
	total	sign	exponent	mantissa
double precision	64	1	11	52 + 1
simple precision	32	1	8	23 + 1

 

IEEE-754: Exponent and Special Values

format	size k	bias b	unbiased		biased	
			e_{min}	e_{max}	e_{min}	e_{max}
SP	8	127 ($= 2^{8-1} - 1$)	-126	127	1	254
DP	11	1023 ($= 2^{11-1} - 1$)	-1022	1023	1	2046

-0	1 00000000 00000000000000000000000000000000
+0	0 00000000 00000000000000000000000000000000
$-\infty$	1 11111111 00000000000000000000000000000000
$+\infty$	0 11111111 00000000000000000000000000000000
NaN	0 11111111 00000000000000000000000000000001 (for instance)


Not a Number (NaN) is the result of **invalid operations** such as $0/0$, $\sqrt{-1}$ or $0 \times \infty$

Basic Cells for Addition

Useful circuit element in computer arithmetic: **counter**

A (m, k) -counter is a cell that counts the number of 1 on its m inputs (result expressed as a k -bit integer)

 
$$\sum_{i=0}^{m-1} a_i = \sum_{j=0}^{k-1} s_j 2^j$$



Standard counters:

- **half-adder** or **HA** is a $(2, 2)$ -counter
- **full-adder** or **FA** is a $(3, 2)$ -counter

FA Cell

 

<i>a</i>	<i>b</i>	<i>d</i>	<i>c</i>	<i>s</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Arithmetic equation:


$$2c + s = a + b + d$$

Logic equation:

$$s = a \oplus b \oplus d$$

$$c = ab + ad + bd$$


Articles about FA in IEEE Journals

 

There many implementations of the FA cell

Carry Ripple Adder (CRA)

 
Very simple architecture: n FA cells connected in **series**




	complexity
delay	$O(n)$
area	$O(n)$

Warning: Sometimes a CRA is also called *Carry Propagate Adder* (CPA), **but** CPA also means a non-redundant adder (that propagates)

Useless Activity in a Carry Ripple Adder

 

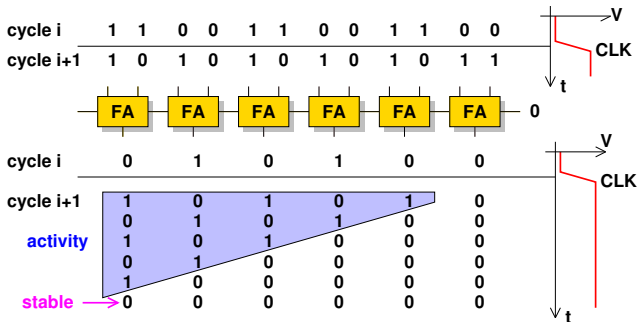Very simple architecture:
 n FA cells connected in series




Theoretical models (equiprobable and uniform distribution of inputs):

- worst case $n^2/2$ transitions
- average $3n/2$ transitions and only $n/2$ useful

Carry-Select Adder

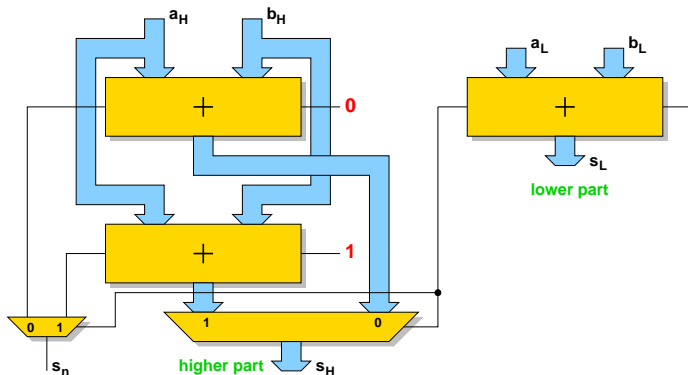Idea: computation of the higher half part for the 2 possible input carries (0 and 1) and selection when the output carry from lower half part is known



Recursive version $\rightarrow O(\log n)$ delay

but there is a fanout problem...

Carry Lookahead Adder

Idea: compute all carries as fast as possible (instead of propagating them)

At rank i , the input carry c_i is 1 in the following cases:


- rank $i - 1$ generates a carry
 $\hookrightarrow g_{i-1} = 1$
- rank $i - 1$ propagates a carry generated at rank $i - 2$
 $\hookrightarrow p_{i-1} = g_{i-2} = 1$
- ranks $i - 1$ and $i - 2$ propagate a carry generated at rank $i - 3$
 $\hookrightarrow p_{i-1} = p_{i-2} = g_{i-3} = 1$
- \vdots
- ranks $i - 1$ to 0 propagate the adder input carry c_0 (set to 1)
 $\hookrightarrow p_{i-1} = p_{i-2} = \dots = p_1 = p_0 = c_0 = 1$

All carries can be computed using the relation ($c_i = g_{i-1} + c_{i-1}p_{i-1}$):

$$c_i = g_{i-1} + p_{i-1}g_{i-2} + p_{i-1}p_{i-2}g_{i-3} + \dots + p_{i-1} \cdots p_1g_0 + p_{i-1} \cdots p_0c_0$$

CLA architecture: parallel evaluation of

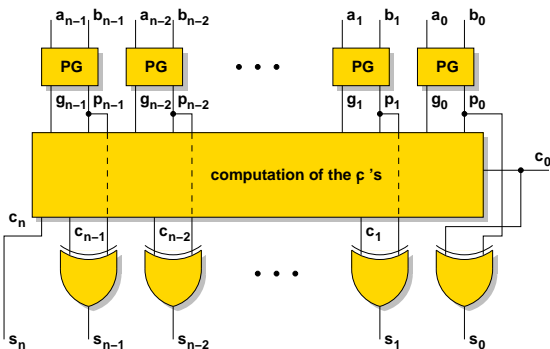- (g_i, p_i) for all i
- carries c_i for all i using the above equation
- sums using $s_i = a_i \oplus b_i \oplus c_i = p_i \oplus c_i$




Carry Lookahead Adder: 4-Bit Example

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$
 
$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$



Parallel-Prefix Problems

The n outputs $(y_{n-1}, y_{n-2}, \dots, y_0)$ are computed using the n inputs $(x_{n-1}, x_{n-2}, \dots, x_0)$ and the **associative operator** \square :


$$y_0 = x_0$$

$$y_1 = x_1 \square x_0$$


$$y_2 = x_2 \square x_1 \square x_0$$

\vdots

 
$$y_{n-1} = x_{n-1} \square x_{n-2} \square \dots \square x_1 \square x_0$$



 
Parallel-Prefix Addition: Standard Architectures




carry ripple

 


Brent-Kung

 

Kogge-Stone

 

Sklansky

 

Han-Carlson

Redundant or Constant Time Adders

To speed-up the addition, one solution consists in “saving” the carries and using them (this makes sense only in case of multiple additions)

In 1961, Avizienis suggested to represent numbers in radix β with digits in $\{-\alpha, -\alpha + 1, \dots, 0, \dots, \alpha - 1, \alpha\}$ instead of $\{0, 1, 2, \dots, \beta - 1\}$ with $\alpha \leq \beta - 1$


Using this representation, if $2\alpha + 1 > \beta$ some numbers have several possible representation at the bit level. For instance, the value 2345 (in the standard representation) can be represented in radix 10 with digits in $\{-5, -4, -3, -2, -1, 0, 1, 2, 3, 4, 5\}$ by the values 2345, 235(-5) or 24(-5)(-5)

Such a representation is said **redundant**

In a redundant number system there is constant-time addition algorithm (without carry propagation) where all computations are done in parallel

Addition


Q: How can we speed up addition?

 

Addition

Q: How can we speed up addition?


R: **Save** the carries!

 

Addition

Q: How can we speed up addition?

R: Save the carries!

 

$$X + Y + Z = S + R = \sum_{i=0}^n (s_i + r_i) 2^i$$

The computation time does not depend on n




$$T(n) = O(1)$$

Addition using the *carry-save* representation

Q: How can we speed up addition?

R: **Save** the carries!

 


$$\begin{aligned} X + Y + Z &= S + R = \sum_{i=0}^n (s_i + r_i) 2^i \\ &= W = \sum_{i=0}^n w_i 2^i \quad \text{avec } w_i = s_i + r_i \in \{0, 1, 2\} \end{aligned}$$

The computation time does **not depend** on n \rightarrow $T(n) = O(1)$

Addition using the *carry-save* representation

Q: How can we speed up addition?

R: **Save** the carries!

 


$$X + Y + Z = S + R = \sum_{i=0}^n (s_i + r_i) 2^i$$

$$= W = \sum_{i=0}^n w_i 2^i \quad \text{avec} \quad w_i = s_i + r_i \in \{0, 1, 2\}$$

$$= \left(w_n w_{n-1} \dots w_1 w_0 \right)_{cs} = \left(\begin{array}{|c|c|} \hline s_n & r_n \\ \hline \end{array} \begin{array}{|c|c|} \hline s_{n-1} & r_{n-1} \\ \hline \end{array} \dots \begin{array}{|c|c|} \hline s_1 & r_1 \\ \hline \end{array} \begin{array}{|c|c|} \hline s_0 & r_0 \\ \hline \end{array} \right)_{cs}$$

The computation time does **not depend** on n \rightarrow $T(n) = O(1)$

Addition of 2 Carry-Save Numbers

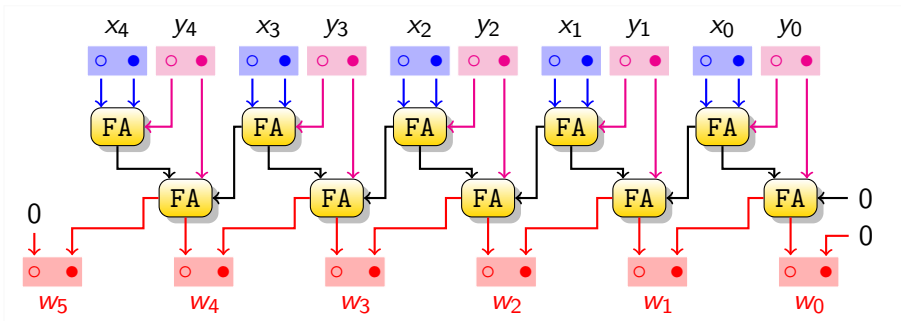


$$X = \sum_{i=0}^n x_i 2^i \quad \text{avec} \quad x_i = x_{s,i} + x_{r,i} = \circ + \bullet$$

$$Y = \sum_{i=0}^n y_i 2^i \quad \text{avec} \quad y_i = y_{s,i} + y_{r,i} = \circ + \bullet$$

$$X+Y = W = \sum_{i=0}^n w_i 2^i \quad \text{avec} \quad w_i = w_{s,i} + w_{r,i} = \circ + \bullet$$

Carry-Save Trees

Example with 3 inputs: A , B and C

 

Carry-save reduction tree: $n(h)$ non-redundant inputs can be reduced by a h -level carry-save tree where $n(h) = \lfloor 3n(h-1)/2 \rfloor$ and $n(0) = 2$

h	1	2	3	4	5	6	7	8	9	10	11
$n(h)$	3	4	6	9	13	19	28	42	63	94	141

Shift-And-Add Multiplication

The product $P = A \times B$ can be performed using additions and shifts with the following (parallel-serial) algorithm:

```
1  $P \leftarrow 0$ 
2 for  $i$  from 0 to  $n - 1$  do
3    $P \leftarrow P + a_i B 2^i$ 
```


Remark: This algorithm requires a **shifter** operator (variable shift amount)

Simplification (constant shift):

```
1  $P \leftarrow 0$ 
2 for  $i$  from 0 to  $n - 1$  do
3    $P \leftarrow (P + a_i B) \times 2^{-1}$ 
4  $P \leftarrow P 2^n$ 
```

Operation on line **4** is virtual

 
Shift-And-Add Multiplication: Implementation



	complexity
delay	$O(n)$
area	$O(n)$


Fast Multipliers

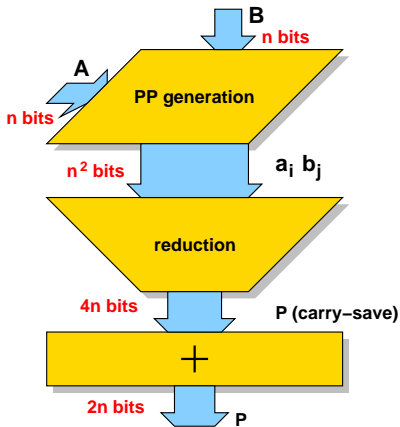1. partial products generation $a_i b_j$
(with or without recoding)
 \hookrightarrow delay in $O(1)$ (fanout a_i, b_j)
 $O(\log n)$
2. sum of the partial products using a *carry-save* reduction tree
 \hookrightarrow delay in $O(\log n)$
3. assimilation of the carries using a fast adder
 \hookrightarrow delay in $O(\log n)$



Multiplication delay $O(\log n)$, area $O(n^2)$

Power Consumption in Fast Multipliers

 


- 30% to 70% of redundant transitions (useless)
- place and route steps based on the internal arrival time
- add a pipeline stage

MAC and FMA

MAC: multiply and accumulate $P(t) = A \times B + P(t - 1)$


A, B are n -bit values and P a m -bit with $m \gg n$ (e.g.,
 $16 \times 16 + 40 \rightarrow 40$ in some DSPs)

 FMA: fused multiply and add $P = A \times B + C$ where A, B, C and P can be stored in different registers




Squarer
 
$$\begin{array}{r} \times \\ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0 \\ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0 \end{array}$$




$$a_i a_i = a_i$$

$$a_i a_j + a_j a_i = 2a_i a_j$$

 
 
$$\begin{aligned} a_i a_j + a_i &= 2a_i a_j + a_i - a_i a_j \\ &= 2a_i a_j + a_i (1 - a_j) \\ &= 2a_i a_j + a_i \bar{a}_j \end{aligned}$$



15 AND + 5 IAND12
3 FA + 2 HA



1 ADD(9 bits)

Multiplication by Constants (1/2)

Problem: substitute a complete multiplier by an optimized sequence of shifts and additions and/or subtractions

Example: $p = 111463 \times x$

algo.	$p = 111463 \times x =$	#op.
direct	$(x \ll 16) + (x \ll 15) + (x \ll 13) + (x \ll 12) + (x \ll 9) + (x \ll 8) + (x \ll 6) + (x \ll 5) + (x \ll 2) + (x \ll 1) + x$	10 \pm
CSD	$(x \ll 17) - (x \ll 14) - (x \ll 12) + (x \ll 10) - (x \ll 7) - (x \ll 5) + (x \ll 3) - x$	7 \pm
Bernstein	$((t_2 \ll 2) + x) \ll 3 - x$ where $t_1 = ((x \ll 3) - x) \ll 2 - x$ $t_2 = t_1 \ll 7 + t_1$	5 \pm
Our	$(t_2 \ll 12) + (t_2 \ll 5) + t_1$ where $t_1 = (x \ll 3) - x$ $t_2 = (t_1 \ll 2) - x$	4 \pm

CSD: canonical signed digit, $111463 = 11011001101100111_2 = 100\bar{1}0\bar{1}0100\bar{1}0\bar{1}0100\bar{1}_2$

Multiplication by Constants (2/2)

Power savings: 30 up to 60%

operator	init.	[1]	[2]	our
DCT 8b	300	94	73	56
DCT 12b	368	100	84	70
DCT 16b	521	129	114	89
DCT 24b	789	212	—	119

Power savings: 10%

operator	init.	[1]	[2]	our
8×8 Had.	56	24	—	24
(16, 11) R.-M.	61	43	31	31
(15, 7) BCH	72	48	47	44
(24, 12, 8) Golay	76	—	47	45


Power savings: up to 40%

operator	init.	[22]	our
8 bits	35	32	24
16 bits	72	70	46


Parks-McClellan filter

`remez(25, [0 0.2 0.25 1], [1 1 0 0]).`


FIR (1, 5, 5, 1)

 


A

 


B

 

C

 

D

 

E


Example: \sqrt{x} over $[1, 2]$ and $\mu \leq 8$ sb

Selection of coefficients leading to sparse recodings

$$p^* = 1.00076383 + 0.48388463x - 0.071198745x^2$$

$$p = 1 + (0.10000\bar{1})_2 x - (0.0001001)_2 x^2$$

 replace \times by a **small** number of \pm



solution	area	period	#cycles	latency	power
wo. tools	1.00	1.00	2	1.00	1.00
w. tools	0.59	0.97	1	0.48	0.45

Modular Exponentiation for RSA

Computation of operations such as : $a^b \bmod n$

$$a^b = \underbrace{a \times a \times a \times a \times \dots \times a \times a \times a}_{a \text{ appears } b \text{ times}}$$

Order of magnitude of exponents: $2^{\text{size of exponent}} \rightsquigarrow 2^{2048} \dots 2^{4096}$

Fast exponentiation principle:

$$\begin{aligned} a^b &= (a^2)^{\frac{b}{2}} && \text{when } b \text{ is even} \\ &= a \times (a^2)^{\frac{b-1}{2}} && \text{when } b \text{ is odd} \end{aligned}$$

Least significant bit of the exponent: bit = 0 \rightsquigarrow even and bit = 1 \rightsquigarrow odd

Square and Multiply Algorithm

input: a, b, n where $b = (b_{t-1}b_{t-2} \dots b_1b_0)_2$

output: $a^b \bmod n$

```
 $r = 1$   
for  $i$  from 0 to  $t - 1$  do  
    if  $b_i = 1$  then  
         $r = r \cdot a \bmod n$   
    endif  
     $a = a^2 \bmod n$   
endfor  
return  $r$ 
```

This is the right to left version (there exists a left to right one)

Elliptic Curve Cryptography in 1 Slide...

protocol level

encryption

signature

etc

$[k]P$

curve level

$ADD(P, Q)$

$P + P$

$DBL(P)$


field level

$x \pm y$

$x \times y$

...

 Elliptic Curve Cryptography in 1 Slide...



$E : y^2 = x^3 + 4x + 20$ over \mathbb{F}_{1009}
points: \mathbf{P} , $\mathbf{Q} = (x, y)$ or (x, y, z) or ...

protocol level

encryption

signature

etc

$[k]\mathbf{P}$

curve level

ADD(\mathbf{P} , \mathbf{Q})

$\mathbf{P} + \mathbf{P}$

DBL(\mathbf{P})


field level

$x \pm y$

$x \times y$

...

 Elliptic Curve Cryptography in 1 Slide...



$E : y^2 = x^3 + 4x + 20$ over \mathbb{F}_{1009}

points: $\mathbf{P}, \mathbf{Q} = (x, y)$ or (x, y, z) or ...

coordinates: $x, y, z \in \mathbb{F}_q$

$\mathbb{F}_p, \mathbb{F}_{2^m}, t : 200-600$ bits

$k = (k_{t-1}k_{t-2} \dots k_1k_0)_2 \in \mathbb{N}$

protocol level

encryption

signature

etc

$[k]\mathbf{P}$

curve level

ADD(\mathbf{P}, \mathbf{Q})

$\mathbf{P} + \mathbf{P}$

DBL(\mathbf{P})


field level

$x \pm y$

$x \times y$

...

 Elliptic Curve Cryptography in 1 Slide...



$E : y^2 = x^3 + 4x + 20$ over \mathbb{F}_{1009}

points: $\mathbf{P}, \mathbf{Q} = (x, y)$ or (x, y, z) or ...

coordinates: $x, y, z \in \mathbb{F}_q$

$\mathbb{F}_p, \mathbb{F}_{2^m}, t : 200-600$ bits

$k = (k_{t-1}k_{t-2} \dots k_1k_0)_2 \in \mathbb{N}$

encryption

signature

etc

$[k]\mathbf{P}$

Scalar multiplication operation

for i from 0 to $t-1$ do


if $k_i = 1$ then $\mathbf{Q} = \text{ADD}(\mathbf{P}, \mathbf{Q})$

$\mathbf{P} = \text{DBL}(\mathbf{P})$


protocol level

curve level

field level

 

 Elliptic Curve Cryptography in 1 Slide...



$$E : y^2 = x^3 + 4x + 20 \text{ over } \mathbb{F}_{1009}$$

points: $\mathbf{P}, \mathbf{Q} = (x, y)$ or (x, y, z) or ...

coordinates: $x, y, z \in \mathbb{F}_q$

$\mathbb{F}_p, \mathbb{F}_{2^m}, t : 200\text{--}600$ bits

$$k = (k_{t-1}k_{t-2} \dots k_1k_0)_2 \in \mathbb{N}$$

protocol level
curve level
field level

encryption

signature

etc

$[k]\mathbf{P}$

ADD(\mathbf{P}, \mathbf{Q})

$\mathbf{P} + \mathbf{P}$

DBL(\mathbf{P})

$x \pm y$

$x \times y$

...

Scalar multiplication operation

for i from 0 to $t-1$ do

if $k_i = 1$ then $\mathbf{Q} = \text{ADD}(\mathbf{P}, \mathbf{Q})$
 $\mathbf{P} = \text{DBL}(\mathbf{P})$


Point addition/doubling operations

sequence of finite field operations

DBL: $v_1 = z_1^2, v_2 = x_1 - v_1, \dots$

ADD: $w_1 = z_1^2, w_2 = z_1 \times w_1, \dots$

 Elliptic Curve Cryptography in 1 Slide...



$$E : y^2 = x^3 + 4x + 20 \text{ over } \mathbb{F}_{1009}$$

points: $\mathbf{P}, \mathbf{Q} = (x, y)$ or (x, y, z) or ...

coordinates: $x, y, z \in \mathbb{F}_q$

$\mathbb{F}_p, \mathbb{F}_{2^m}, t : 200\text{--}600$ bits

$k = (k_{t-1}k_{t-2}\dots k_1k_0)_2 \in \mathbb{N}$

protocol level

encryption
signature
etc

$[k]\mathbf{P}$

Scalar multiplication operation
for i from 0 to $t-1$ do
 if $k_i = 1$ then $\mathbf{Q} = \text{ADD}(\mathbf{P}, \mathbf{Q})$
 $\mathbf{P} = \text{DBL}(\mathbf{P})$

curve level

$\text{ADD}(\mathbf{P}, \mathbf{Q})$

$\mathbf{P} + \mathbf{P}$
 $\text{DBL}(\mathbf{P})$

Point addition/doubling operations
sequence of finite field operations
 $\text{DBL}: v_1 = z_1^2, v_2 = x_1 - v_1, \dots$
 $\text{ADD}: w_1 = z_1^2, w_2 = z_1 \times w_1, \dots$

field level

$x \pm y$


$x \times y$

...


\mathbb{F}_p or \mathbb{F}_{2^m} operations
operation modulo large prime (\mathbb{F}_p)
or irreducible polynomial (\mathbb{F}_{2^m})

Introduction to Physical Attacks


Attacks

 

Attacks

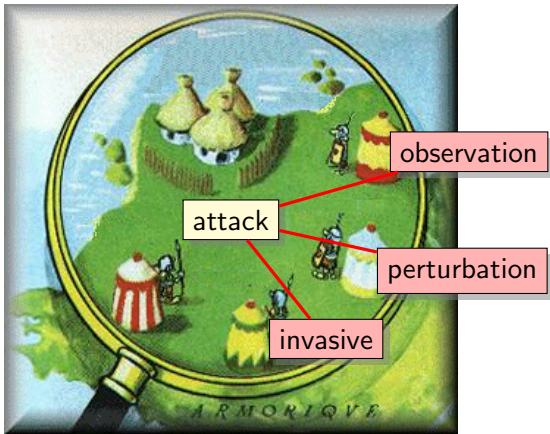


Attacks

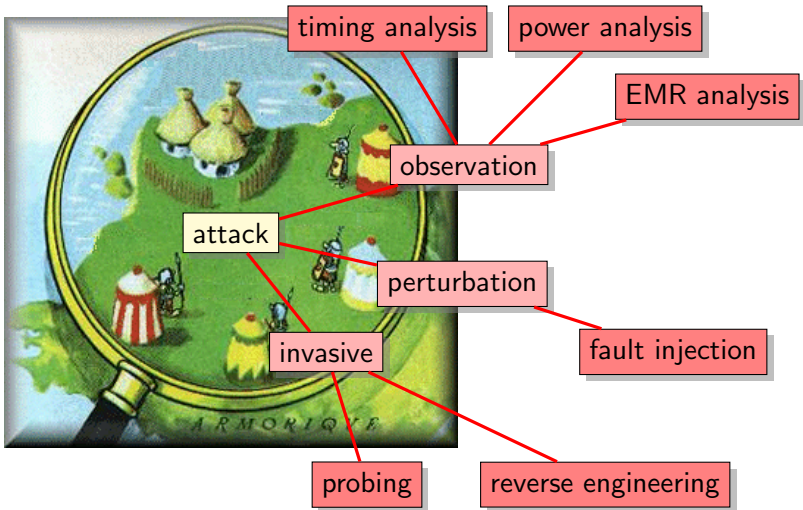


EMR = Electromagnetic radiation

Attacks

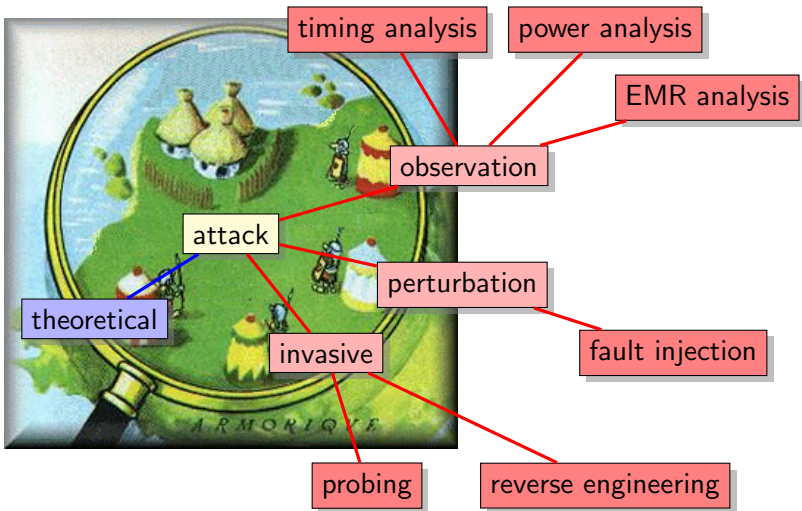

EMR = Electromagnetic radiation

Attacks

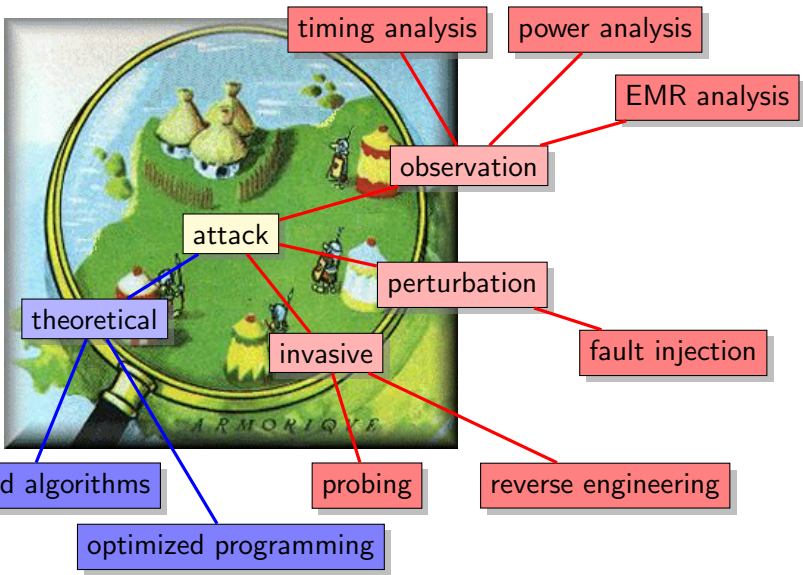

EMR = Electromagnetic radiation

Side Channel Attacks (SCAs) (1/2)

Attack: attempt to find, **without** any knowledge about the secret:


- the message (or parts of the message)
- informations on the message
- the secret (or parts of the secret)

Side Channel Attacks (SCAs) (1/2)


Attack: attempt to find, **without** any knowledge about the secret:

- the message (or parts of the message)
- informations on the message
- the secret (or parts of the secret)

“Old style” side channel attacks:

 


Side Channel Attacks (2/2)

 

General principle: measure **external parameter(s)** on running device in order to deduce **internal informations**

Side Channel Attacks (2/2)

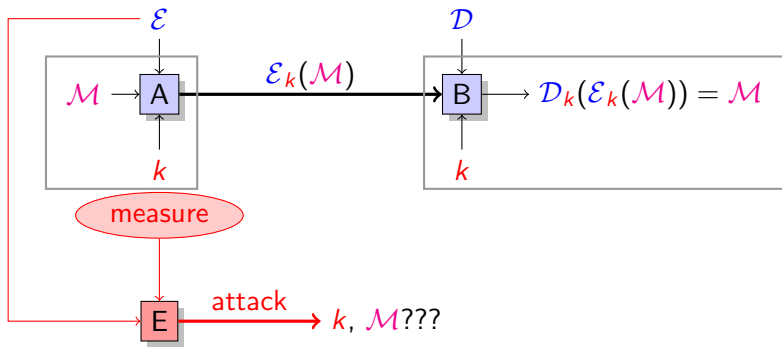

General principle: measure external parameter(s) on running device in order to deduce internal informations

What Should be Measured?

Answer: **everything** that can “enter” and/or “get out” in/from the device

- power consumption
- electromagnetic radiation
- temperature
- sound
- computation time
- number of cache misses
- number and type of error messages
- ...


The measured parameters may provide informations on:

- **global** behavior (temperature, power, sound...)
- **local** behavior (EMR, # cache misses...)


Power Consumption Analysis

General principle:

 1. measure the current $i(t)$ in the cryptosystem
2. use those measurements to “deduce” secret informations




“Read” the Traces

 

Source: [8] Kocher, Jaffe and Jun. **Differential Power Analysis**, Crypto99

"Read" the Traces

 

- algorithm → decomposition into steps
- detect loops
 - ▶ constant time for the loop iterations
 - ▶ non-constant time for the loop iterations

Source: [8] Kocher, Jaffe and Jun. **Differential Power Analysis**, Crypto99

Differences & External Signature

An algorithm


:

```
 $r = c_0$   
for  $i$  from 1 to  $n$  do  
  if  $a_i = 0$  then  
     $r = r + c_1$   
  else  
     $r = r \times c_2$ 
```

Differences & External Signature

An algorithm has a **current signature** :

 
```
 $r = c_0$   
for  $i$  from 1 to  $n$  do  
  if  $a_i = 0$  then  
     $r = r + c_1$   
  else  
     $r = r \times c_2$ 
```




Differences & External Signature

An algorithm has a **current signature** and a **time signature**:
 
```
r = c0
for i from 1 to n do
  if ai = 0 then
    r = r + c1
  else
    r = r × c2
```




Simple Power Analysis (SPA)

 

Source: [8]

Simple Power Analysis (SPA)

 

Source: [8]


SPA in Practice

General principle:

algorithm


SPA in Practice

General principle:

 


SPA in Practice

General principle:

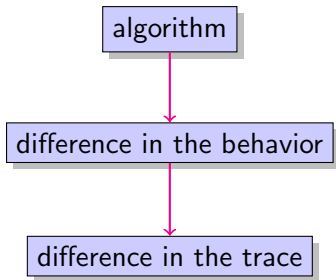


SPA in Practice

General principle:

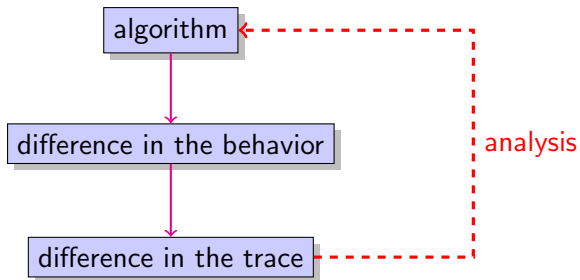

SPA in Practice

General principle:

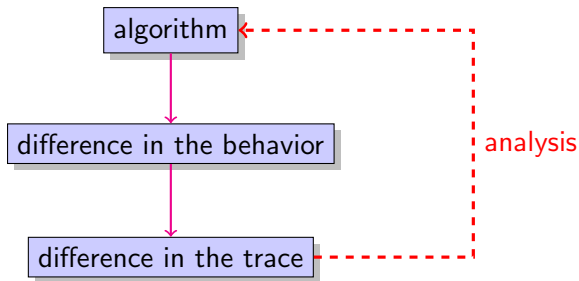


Methods: interpretation of the differences in

- control signals
- computation time
- operand values
- ...


Limits of the SPA

 Example of behavior difference: (activity into a register)




Limits of the SPA

 Example of behavior difference: (activity into a register)



Limits of the SPA

 Example of behavior difference: (activity into a register)




Important: a small difference may be evaluated has a **noise** during the measurement → traces cannot be distinguished

Question: what can be done when differences are too small?

Limits of the SPA

 Example of behavior difference: (activity into a register)



Important: a small difference may be evaluated has a **noise** during the measurement → traces cannot be distinguished


Question: what can be done when differences are too small?

Answer: use **statistics** over **several** traces


Differential Power Analysis (DPA)

cryptosystem


Differential Power Analysis (DPA)

 


Differential Power Analysis (DPA)

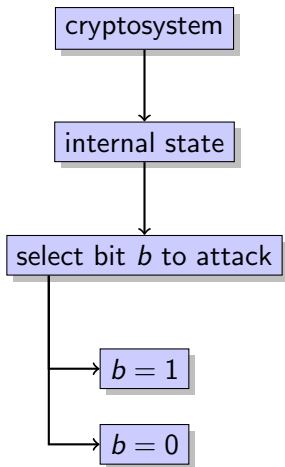


Differential Power Analysis (DPA)

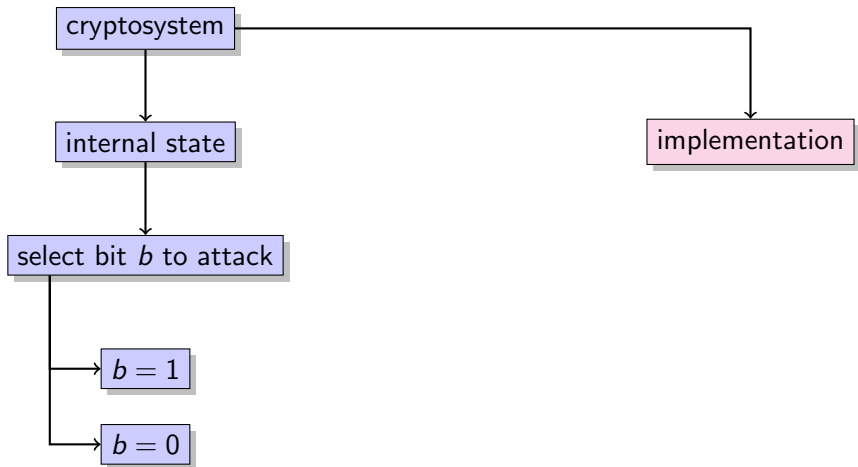


Differential Power Analysis (DPA)

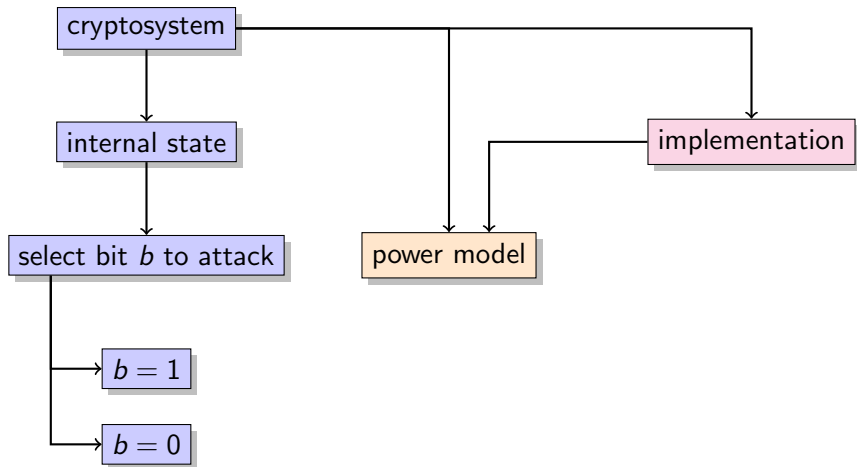


Differential Power Analysis (DPA)

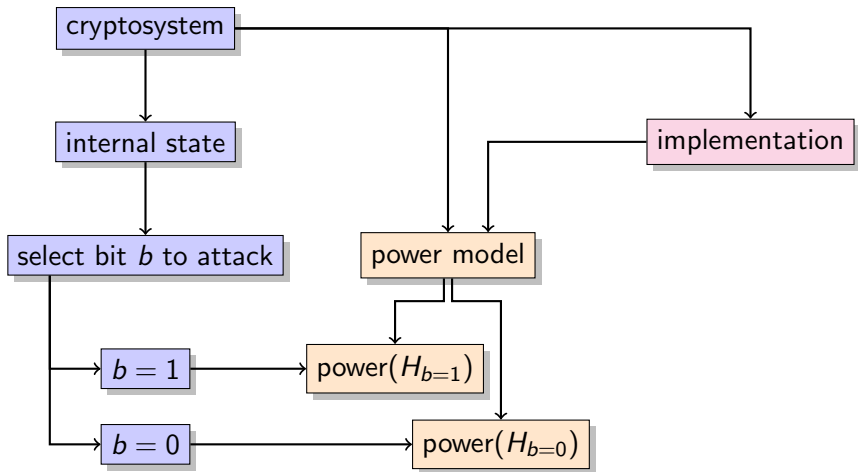


Differential Power Analysis (DPA)

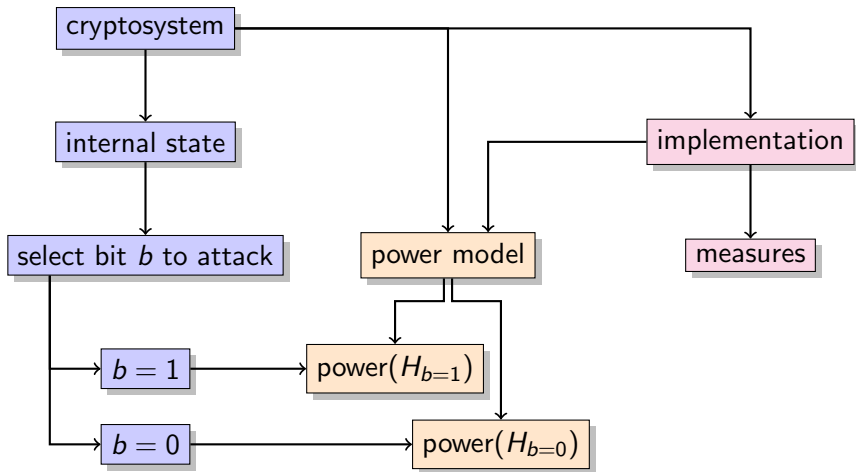

Differential Power Analysis (DPA)

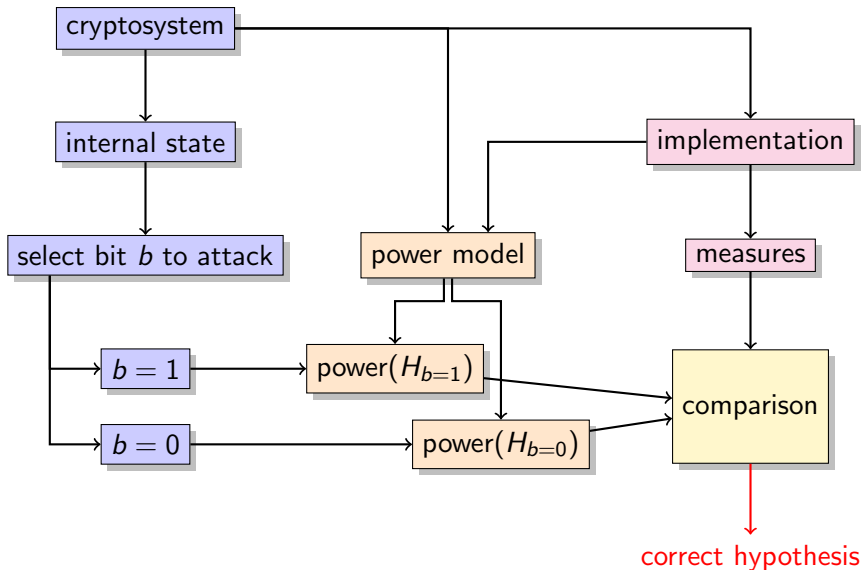

 
Differential Power Analysis (DPA) Example



Template Attack

cryptosystem

Template Attack

 

Template Attack

cryptosystem

internal state


select variable v to attack

$v = 0$


$v = 1$

$v = 2$


Template Attack

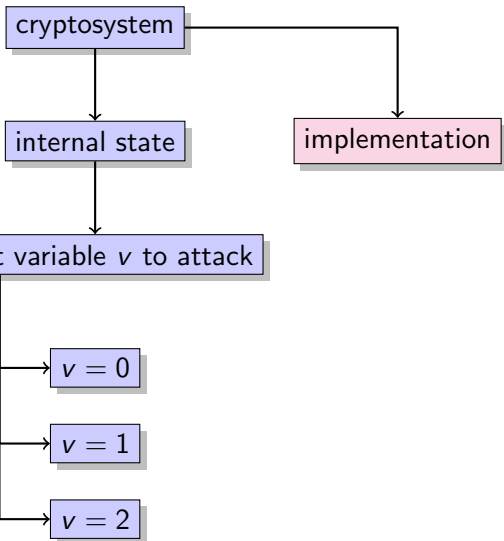


Template Attack

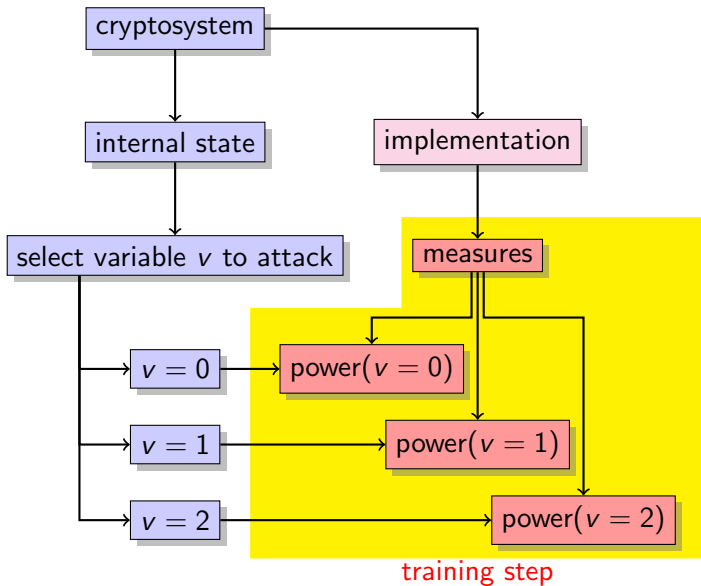

Template Attack

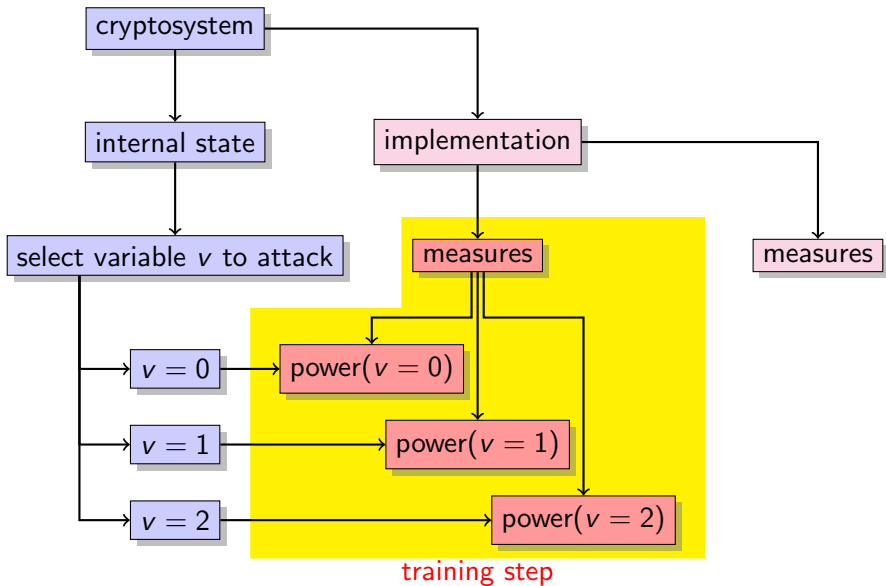


Template Attack

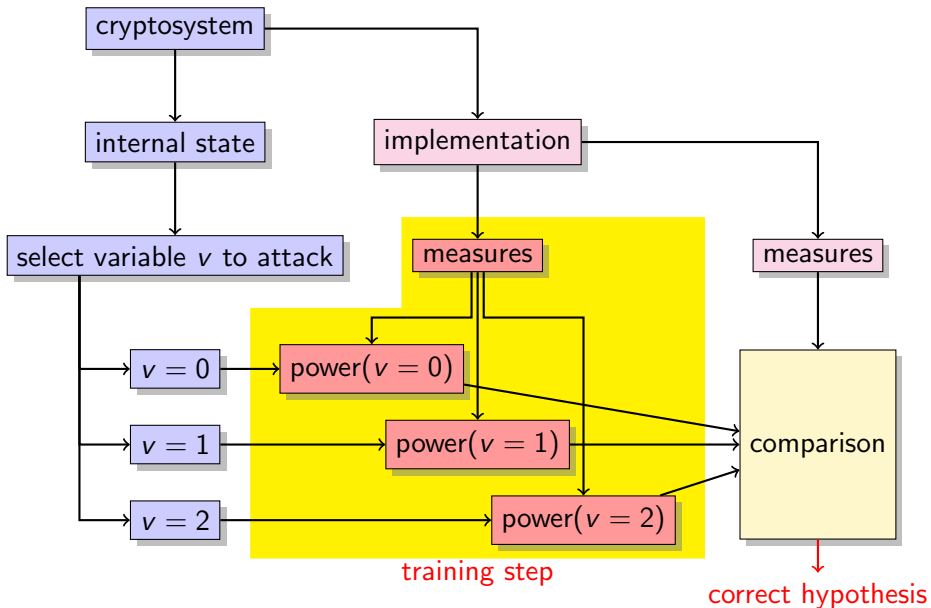

Electromagnetic Radiation Analysis (1/2)

 
General principle: use a **probe** to measure the EMR



EMR measurement:

Electromagnetic Radiation Analysis (1/2)

 General principle: use a **probe** to measure the EMR




EMR measurement:

- **global** EMR with a **large probe**

Electromagnetic Radiation Analysis (1/2)

 General principle: use a **probe** to measure the EMR



EMR measurement:

- **global** EMR with a **large probe**
- **local** EMR with a **micro-probe**

Electromagnetic Radiation Analysis (2/2)

EMR analysis methods:


- simple electromagnetic analysis: SEMA
- differential electromagnetic analysis: DEMA

Local EMR analysis may be used to determine internal architecture details, and then select weak parts of the circuit for the attack

→ X-Y table



Side Channel Attack on ECC

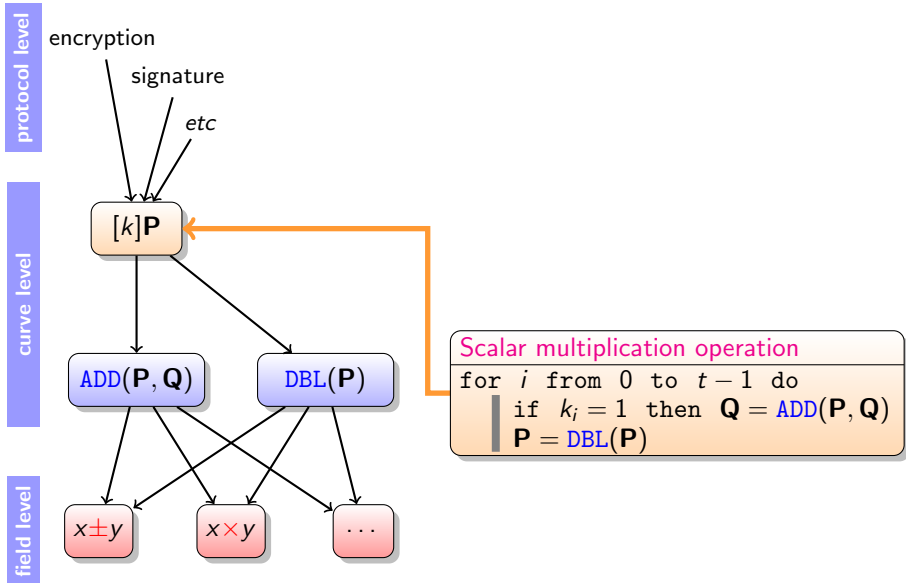

Side Channel Attack on ECC

protocol level

encryption

signature

etc

$[k]P$

curve level

$ADD(P, Q)$


$DBL(P)$

field level

$x \pm y$

$x \times y$

...

 

Scalar multiplication operation

```
for  $i$  from 0 to  $t-1$  do
  if  $k_i = 1$  then  $Q = ADD(P, Q)$ 
   $P = DBL(P)$ 
```

Side Channel Attack on ECC

protocol level

encryption

signature

etc

$[k]P$

curve level

$ADD(P, Q)$


$DBL(P)$

field level

$x \pm y$

$x \times y$



...

 

Scalar multiplication operation

```
for i from 0 to t-1 do
  if  $k_i = 1$  then  $Q = ADD(P, Q)$ 
   $P = DBL(P)$ 
```



Side Channel Attack on ECC

  

Scalar multiplication operation

```
for  $i$  from 0 to  $t-1$  do  
    if  $k_i = 1$  then  $Q = \text{ADD}(P, Q)$   
     $P = \text{DBL}(P)$ 
```

Side Channel Attack on ECC

 
 


Scalar multiplication operation

```
for  $i$  from 0 to  $t-1$  do  
    if  $k_i = 1$  then  $Q = \text{ADD}(P, Q)$   
     $P = \text{DBL}(P)$ 
```

- simple power analysis (& variants)

Side Channel Attack on ECC

  

Scalar multiplication operation

```
for  $i$  from 0 to  $t-1$  do  
    if  $k_i = 1$  then  $Q = ADD(P, Q)$   
     $P = DBL(P)$ 
```

- simple power analysis (& variants)
- differential power analysis (& variants)
- horizontal/vertical/templates/... attacks

Protections at the Arithmetic Level

Countermeasure

Principles for preventing attacks:

- **embed** additional **protection blocks**
- **modify** the original circuit into a **secured** version
- application levels: circuit, architecture, algorithm, protocol. . .

Countermeasure

Principles for preventing attacks:


- **embed** additional **protection blocks**
- **modify** the original circuit into a **secured** version
- application levels: circuit, architecture, algorithm, protocol. . .

Countermeasures:

- electrical shielding
- detectors, estimators, decoupling
- use uniform computation durations and power consumption
- use detection/correction codes (for fault injection attacks)
- provide a random behavior (algorithms, representation, operations. . .)
- add noise (e.g. masking, useless instructions/computations)
- circuit reconfiguration (algorithms, block location, representation of values. . .)


Low-Level Coding and Circuit Activity

Assumptions:



- b is a bit (i.e. $b \in \{0, 1\}$, logical or mathematical value)
- electrical states for a wire  : V_{DD} (logical 1) or GND (logical 0)

Low-Level Coding and Circuit Activity

Assumptions:


- b is a bit (i.e. $b \in \{0, 1\}$, logical or mathematical value)
- electrical states for a wire  : V_{DD} (logical 1) or GND (logical 0)

Low-level codings of a bit:







	$b = 0$	$b = 1$
standard	 GND	 V_{DD}

Low-Level Coding and Circuit Activity

Assumptions:

- b is a bit (i.e. $b \in \{0, 1\}$, logical or mathematical value)
- electrical states for a wire  : V_{DD} (logical 1) or GND (logical 0)

Low-level codings of a bit:

	$b = 0$	$b = 1$
standard	 GND	 V_{DD}
dual rail	 $r_0 = V_{DD}$  $r_1 = \text{GND}$] $(1, 0)_{\text{DR}}$	 $r_0 = \text{GND}$  $r_1 = V_{DD}$] $(0, 1)_{\text{DR}}$


Low-Level Coding and Circuit Activity

Assumptions:

- b is a bit (i.e. $b \in \{0, 1\}$, logical or mathematical value)
- electrical states for a wire ————— : V_{DD} (logical 1) or GND (logical 0)

Low-level codings of a bit:

	$b = 0$	$b = 1$
standard	————— GND	————— V_{DD}
dual rail	————— $r_0 = V_{DD}$ ————— $r_1 = \text{GND}$] $(1, 0)_{DR}$	————— $r_0 = \text{GND}$ ————— $r_1 = V_{DD}$] $(0, 1)_{DR}$

 


Low-Level Coding and Circuit Activity

Assumptions:

- b is a bit (i.e. $b \in \{0, 1\}$, logical or mathematical value)
- electrical states for a wire ————— : V_{DD} (logical 1) or GND (logical 0)

Low-level codings of a bit:

	$b = 0$	$b = 1$
standard	————— GND	————— V_{DD}
dual rail	————— $r_0 = V_{DD}$ ————— $r_1 = \text{GND}$] $(1, 0)_{\text{DR}}$	————— $r_0 = \text{GND}$ ————— $r_1 = V_{DD}$] $(0, 1)_{\text{DR}}$

 


Circuit Logic Style

Countermeasure principles: **uniformize** circuit activity and **exclusive coding**

Circuit Logic Style

Countermeasure principles: **uniformize** circuit activity and **exclusive coding**

 
Solution based on precharge logic and dual-rail coding:



Circuit Logic Style

Countermeasure principles: **uniformize** circuit activity and **exclusive** coding

 Solution based on precharge logic and dual-rail coding:



Solution based on validity line and dual-rail coding:






Important overhead: silicon area and local storage (registers)

Countermeasure: Architecture


Increase internal parallelism:

   - replace one fast but big operator
- by several instances of a small but slow one




Protected Multipliers

Unprotected

 

Protected Multipliers

Unprotected

 

Protected

Overhead:


Area/time < 10 %

References:


PhD D. Pamula [9]

Articles: [12], [11],

[10]




 


Protected (Old) Accelerator

 

Warning: old dedicated accelerator (similar behavior is expected for our new one)

    Circuit-Level Protections for Arithmetic Operators




References: [5] and [6]

Arithmetic Level Countermeasures

Redundant number system =

 - a way to improve the performance of some operations
- a way to represent a value with different representations



Important property: $\forall i \quad [R_i(k)]P = [k]P$

Proposed solution: use random redundant representations of k

Double-Base Number System

Standard radix-2 representation:

$$k = \sum_{i=0}^{t-1} k_i 2^i = \boxed{k_{t-1} \mid k_{t-2} \mid \cdots \mid k_2 \mid k_1 \mid k_0} \quad t \text{ explicit digits}$$

Double-Base Number System

Standard radix-2 representation:

$$k = \sum_{i=0}^{t-1} k_i 2^i = \begin{array}{|c|c|c|c|c|c|} \hline & 2^{t-1} & 2^{t-2} & \dots & 2^2 & 2^1 & 2^0 \\ \hline & k_{t-1} & k_{t-2} & \dots & k_2 & k_1 & k_0 \\ \hline \end{array} \begin{array}{l} \text{implicit weights} \\ t \text{ explicit digits} \end{array}$$

Digits: $k_i \in \{0, 1\}$, typical size: $t \in \{160, \dots, 600\}$

Double-Base Number System

Standard radix-2 representation:

$$k = \sum_{i=0}^{t-1} k_i 2^i = \begin{array}{|c|c|c|c|c|c|} \hline 2^{t-1} & 2^{t-2} & \dots & 2^2 & 2^1 & 2^0 \\ \hline k_{t-1} & k_{t-2} & \dots & k_2 & k_1 & k_0 \\ \hline \end{array} \begin{array}{l} \text{implicit weights} \\ t \text{ explicit digits} \end{array}$$

Digits: $k_i \in \{0, 1\}$, typical size: $t \in \{160, \dots, 600\}$

Double-Base Number System (DBNS):

$$k = \sum_{j=0}^{n-1} k_j 2^{a_j} 3^{b_j} =$$

Double-Base Number System

Standard radix-2 representation:

$$k = \sum_{i=0}^{t-1} k_i 2^i = \begin{array}{|c|c|c|c|c|c|} \hline 2^{t-1} & 2^{t-2} & \dots & 2^2 & 2^1 & 2^0 \\ \hline k_{t-1} & k_{t-2} & \dots & k_2 & k_1 & k_0 \\ \hline \end{array} \begin{array}{l} \text{implicit weights} \\ t \text{ explicit digits} \end{array}$$

Digits: $k_i \in \{0, 1\}$, typical size: $t \in \{160, \dots, 600\}$

Double-Base Number System (DBNS):

$$k = \sum_{j=0}^{n-1} k_j 2^{a_j} 3^{b_j} = \begin{array}{|c|c|c|c|} \hline k_{n-1} & \dots & k_1 & k_0 \\ \hline a_{n-1} & \dots & a_1 & a_0 \\ \hline b_{n-1} & \dots & b_1 & b_0 \\ \hline \end{array} \begin{array}{l} n \text{ (2, 3)-terms} \\ \text{explicit "digits"} \\ \text{explicit ranks} \end{array}$$

$a_j, b_j \in \mathbb{N}$, $k_j \in \{1\}$ or $k_j \in \{-1, 1\}$, size $n \approx \log t$

Double-Base Number System

Standard radix-2 representation:

$$k = \sum_{i=0}^{t-1} k_i 2^i = \begin{array}{|c|c|c|c|c|c|} \hline 2^{t-1} & 2^{t-2} & \dots & 2^2 & 2^1 & 2^0 \\ \hline k_{t-1} & k_{t-2} & \dots & k_2 & k_1 & k_0 \\ \hline \end{array} \begin{array}{l} \text{implicit weights} \\ t \text{ explicit digits} \end{array}$$

Digits: $k_i \in \{0, 1\}$, typical size: $t \in \{160, \dots, 600\}$

Double-Base Number System (DBNS):

$$k = \sum_{j=0}^{n-1} k_j 2^{a_j} 3^{b_j} = \begin{array}{|c|c|c|c|} \hline k_{n-1} & \dots & k_1 & k_0 \\ \hline a_{n-1} & \dots & a_1 & a_0 \\ \hline b_{n-1} & \dots & b_1 & b_0 \\ \hline \end{array} \begin{array}{l} n \text{ (2, 3)-terms} \\ \text{explicit "digits"} \\ \text{explicit ranks} \end{array}$$

$a_j, b_j \in \mathbb{N}$, $k_j \in \{1\}$ or $k_j \in \{-1, 1\}$, size $n \approx \log t$

DBNS is a very **redundant** and **sparse** representation: $1701 = (11010100101)_2$

$$\begin{aligned} 1701 &= 243 + 1458 &= 2^0 3^5 + 2^1 3^6 &= (1, 0, 5), (1, 1, 6) \\ &= 1728 - 27 &= 2^6 3^3 - 2^0 3^3 &= (1, 6, 3), (-1, 0, 3) \\ &= 729 + 972 &= 2^0 3^6 + 2^2 3^5 &= (1, 0, 6), (1, 2, 5) \\ &\dots \end{aligned}$$

Randomized DBNS Recoding of the Scalar k

On-the-fly DBNS random recoding for the scalar k
randomly recode windows of the scalar k on-the-fly:
 $1 + 2 \Leftrightarrow 3$ $1 + 3 \Leftrightarrow 2^2$ $1 + 2^3 \Leftrightarrow 3^2$...
control number of reductions (\leftarrow) and expansions (\rightarrow)

protocol level

encryption
signature
etc

$[k]P$

curve level

ADD(P, Q)

DBL(P)

TPL(P)


Point tripling operation
 $Q = TPL(P) = P + P + P$

field level

$x \pm y$

$x \times y$

...

 

Randomized DBNS Recoding of the Scalar k

On-the-fly DBNS random recoding for the scalar k

randomly recode windows of the scalar k on-the-fly:

$$1 + 2 \Leftrightarrow 3 \quad 1 + 3 \Leftrightarrow 2^2 \quad 1 + 2^3 \Leftrightarrow 3^2 \quad \dots$$

control number of reductions (\leftarrow) and expansions (\rightarrow)

protocol level

curve level

field level

encryption

signature

etc

$[k]P$

ADD(P, Q)


DBL(P)

TPL(P)

$x \pm y$

$x \times y$

...

 

Point tripling operation

$$Q = \text{TPL}(P) = P + P + P$$

Randomized DBNS Recoding of the Scalar k

On-the-fly DBNS random recoding for the scalar k

randomly recode windows of the scalar k on-the-fly:

$$1 + 2 \Leftrightarrow 3 \quad 1 + 3 \Leftrightarrow 2^2 \quad 1 + 2^3 \Leftrightarrow 3^2 \quad \dots$$

control number of reductions (\leftarrow) and expansions (\rightarrow)

protocol level

encryption
signature
etc

$[k]P$

curve level

ADD(P, Q)

DBL(P)

TPL(P)

Point tripling operation


$$Q = \text{TPL}(P) = P + P + P$$

field level

$x \pm y$

$x \times y$

...

 

DBNS is redundant \Rightarrow security \nearrow

DBNS is sparse \Rightarrow 20–30% speed \nearrow

Ref: [3] Chabrier, Pamula & Tisserand.
Asilomar 2009

References

References I

Surveys: Proc. IEEE 2006 [1], Proc. IEEE 2012 [2], IEEE TVLSI 2013 [7]

- [1] H. Bar-Ei, H. Choukri, D. Naccache, M. Tunstall, and C. Whelan.
The sorcerer's apprentice guide to fault attacks.
Proceedings of the IEEE, 94(2):370–382, February 2006.
- [2] A. Barengi, L. Breveglieri, I. Koren, and D. Naccache.
Fault injection attacks on cryptographic devices: Theory, practice, and countermeasures.
Proceedings of the IEEE, 100(11):3056–3076, November 2012.
- [3] T. Chabrier, D. Pamula, and A. Tisserand.
Hardware implementation of DBNS recoding for ECC processor.
In *Proc. 44rd Asilomar Conference on Signals, Systems and Computers*, pages 1129–1133, Pacific Grove, California, U.S.A., November 2010. IEEE.
- [4] T. Chabrier and A. Tisserand.
On-the-fly multi-base recoding for ECC scalar multiplication without pre-computations.
In A. Nannarelli, P.-M. Seidel, and P. T. P. Tang, editors, *Proc. 21st Symposium on Computer Arithmetic (ARITH)*, pages 219–228, Austin, TX, U.S.A, April 2013. IEEE Computer Society.
- [5] J. Chen, A. Tisserand, E. M. Popovici, and S. Cotofana.
Robust sub-powered asynchronous logic.
In J. Becker and M. R. Adrover, editors, *Proc. 24th International Workshop on Power and Timing Modeling, Optimization and Simulation (PATMOS)*, pages 1–7, Palma de Mallorca, Spain, September 2014. IEEE.
- [6] J. Chen, A. Tisserand, E. M. Popovici, and S. Cotofana.
Asynchronous charge sharing power consistent Montgomery multiplier.
In J. Spaso and E Yahya, editors, *Proc. 21st IEEE International Symposium on Asynchronous Circuits and Systems (ASYNC)*, pages 132–138, Mountain View, California, USA, May 2015.
- [7] D. Karaklajic, J.-M. Schmidt, and I. Verbauwhede.
Hardware designer's guide to fault attacks.
IEEE Transactions on Very Large Scale Integration (VLSI) Systems, 21(12):2295–2306, December 2013.

References II

- [8] P. C. Kocher, J. Jaffe, and B. Jun.
Differential power analysis.
In *Proc. Advances in Cryptology (CRYPTO)*, volume 1666 of *LNCS*, pages 388–397. Springer, August 1999.
- [9] D. Pamula.
Arithmetic Operators on $GF(2^m)$ for Cryptographic Applications: Performance - Power Consumption - Security Tradeoffs.
Phd thesis, University of Rennes 1 and Silesian University of Technology, December 2012.
- [10] D. Pamula, E. Hrynkiewicz, and A. Tisserand.
Analysis of $GF(2^{233})$ multipliers regarding elliptic curve cryptosystem applications.
In *11th IFAC/IEEE International Conference on Programmable Devices and Embedded Systems (PDeS)*, pages 271–276, Brno, Czech Republic, May 2012.
- [11] D. Pamula and A. Tisserand.
 $GF(2^m)$ finite-field multipliers with reduced activity variations.
In *4th International Workshop on the Arithmetic of Finite Fields*, volume 7369 of *LNCS*, pages 152–167, Bochum, Germany, July 2012. Springer.
- [12] D. Pamula and A. Tisserand.
Fast and secure finite field multipliers.
In *Proc. 18th Euromicro Conference on Digital System Design (DSD)*, pages 653–660, Madeira, Portugal, August 2015.
- [13] J. Proy, N. Veyrat-Charvillon, A. Tisserand, and N. Meloni.
Full hardware implementation of short addition chains recoding for ECC scalar multiplication.
In *Actes Conférence d'informatique en Parallélisme, Architecture et Système (CompAS)*, Lille, France, June 2015.

Good Books (in French)

Micro et nano-électronique

Bases, Composants, Circuits

Hervé Fanet

2006

Dunod

ISBN: 2-10-049141-5



Arithmétique des ordinateurs

Jean-Michel Muller

1989

Masson

ISBN: 2-225-81689-1

(web version)

Good Books (in English)

CMOS VLSI Design


A Circuits and Systems Perspective

Neil Weste and David Harris

3rd edition, 2004

Addison Wesley

ISBN: 0-321-14901-7

 

Power Analysis Attacks

Revealing the Secrets of Smart Cards

Stefan Mangard, Elisabeth Oswald and

Thomas Popp

2007

Springer

ISBN:978-0-387-30857-9

Good Books (in English)

Digital Arithmetic

Milos Ercegovac and Tomas Lang

2003

Morgan Kaufmann

ISBN: 1-55860-798-6



Thank you!

Contact (will change in a few months):

- <mailto:arnaud.tisserand@univ-ubs.fr>
- <http://www-labsticc.univ-ubs.fr/~tisseran>